

Analog Weight Perturbation on-chip learning



Maurizio Valle

Feed forward circuit architecture: main features

- Current mode circuits
- Translinear circuits
- Information coding through differential balanced signals
- Low Power / Low Voltage i.e.: *weak inversion region of operation of devices, supply voltage in the range [2.5÷3]V or lower*
- Implementation of normalised sums of currents: *both for the synaptic output currents and the output error (i.e. target - output neuron current) currents;*
- Programmable neuron circuit gain;
- Trade off between power and area i.e.: *the maximum transistor bias current has been set to 500nA.*


M. Valle

Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

1

Feed forward circuit architecture

 

M. Valle


Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

2

WP learning algorithm

- select an input pattern of the learning set
- feed forward phase
- output error computation and storage
(i.e. $\varepsilon_p(w) = \sum (target\ output\ value - neuron\ output\ value)$)
- weights perturbation
- feed forward phase
- perturbed output error computation and storage
(i.e. $\varepsilon_p(w+p) = \sum (target\ output\ value - neuron\ output\ value)$)
- “measurement” of the error gradient $\Delta \varepsilon_p$
(in terms of the absolute value and sign)
- back propagation to all synapses of the two signals: absolute value and sign of $\Delta \varepsilon_p$
- weights update: $w = w + \Delta w$
- if $\varepsilon_p(w) > given\ threshold$ goto point 1
else if end

 


M. Valle

Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning


3

 Circuits blocks common to the whole architecture




$$\Delta w_{ij} \cong -\eta \frac{\varepsilon(w + p_{ij}^{(n)}) - \varepsilon(w_{ij})}{p_{ij}^{(n)}}$$

 Analog circuit MLP architecture with on-chip WP learning



Circuit design criteria




- The current-mode circuit design approach $\rightarrow$ **Current mirrors, multipliers, adders**
- Information coding through differential balanced signals $\rightarrow$ **linearity increase and noise minimization**
- Current signals distribution $\rightarrow$
- Current signals normalization $\rightarrow$
- The translinear principle (multiplier)
 - The gm/Id design methodology $\rightarrow$ $\frac{I_{DS}}{W} \leq 6.25 \cdot 10^{-3} \left[\frac{A}{m} \right]$
- Bandwidth requirements $\rightarrow$ $\frac{I_{DS}}{W} \geq 2/7 \cdot 10^{-3} \left[\frac{A}{m} \right]$
- Translinear loop devices sizes $\rightarrow$ $I_{DS} \approx 10^{-8} A$ and $W \approx 10^{-5} m$ $\rightarrow$ $I_{DS} = 250 nA$ and $W = 40 \mu m$.

 

The input transconductor (block G)


- I_G in the range $[-250nA \div 250nA]$
- The cut-off frequency is about 1MHz.
- THD of I_G : V_{in} input sinusoidal voltage signal with 200mV peak to peak

10KHz	100KHz	1MHz
0.8%	1.5%	3.2%

   

Weight Transconductor

 - The linearity range of single ended to differential block is greater than “traditional” transconductor
- The symmetrical balanced voltages in input to transconductor permit to have right asymptotes $[-250\text{nA}; 250\text{nA}]$.



M. Valle

Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

8

Single ended to differential block

Suppose M_i ($i=1..4$) equal MOS in saturation region:

$$I_{M1} = I_{M3}, \text{ i.e.:}$$

$$K[(V_p - V_{in}) - V_{th}] = K[(V_{dd} - V_p) - V_{th}] \text{ and so}$$

$$V_p = \frac{1}{2}(V_{dd} + V_{in})$$

$$\text{At the same time, } I_{M2} = I_{M4}, \text{ i.e.:}$$


$$K[(V_{dd} - V_p) - V_{th}] = K[V_m - V_{th}] \text{ and so}$$

$$V_m = \frac{1}{2}(V_{dd} - V_{in})$$

$$V_{sum} = V_p + V_m = V_{dd}$$

$$V_{diff} = V_p - V_m = V_{in}$$

 V_p and V_m are differential balanced voltage



M. Valle


Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

9

The synaptic circuit (block S)

 - In the design of the synapse we have to take into account:
 - the circuitry necessary to perform the feed-forward phase and,
 - the learning circuitry necessary for the perturbation and the update of the weight voltage in according to the Weight Perturbation algorithm.




M. Valle

Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

10

 
The synaptic circuit: weight perturbation (block WP)



- if **pert="low"**
 - Negative perturbation, i.e.
 $V_W^k \text{ perturbed} = V_W^k - \Delta V_{W \text{ pert}}$

- if **pert="high"**
 - Positive perturbation, i.e.
 $V_W^k \text{ perturbed} = V_W^k + \Delta V_{W \text{ pert}}$
 
$$\Delta V_{W \text{ pert}} = \frac{V_{step}}{11}$$



Inputs		Outputs			Note
Enable_pert	V _{pert}	NoPert	PositivePert	NegativePert	
0	X	1	1	0	No perturbation
1	0	0	1	1	Negative Perturbation
1	1	0	0	0	Positive Perturbation


M. Valle

Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

11

 The synaptic circuit: weight update (block WU)



Taking into account:

$$\Delta W_{ji}^l = -\eta' \cdot \Delta \varepsilon_p \cdot \text{pert}_{ji}^l \quad \eta' = -\frac{\eta}{\text{step}}$$

$$\text{pert}_{ji}^l = \begin{cases} +1 \\ -1 \end{cases} \text{ With equal probability}$$

$$l \in [1 + N] \quad j \in [1 + n^l] \quad i \in [1 + n^{l-1}]$$

Inputs			Outputs		Note
Enable_update	V _{perij}	V _{sign}	Increase	Decrease	
0	X	X	1	0	No update
1	0	0	1	1	Weight Decrement
1	0	1	0	0	Weight Increment
1	1	0	0	0	Weight Increment
1	1	1	1	1	Weight Decrement

M. Valle



Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

12

The subtract and ABS circuit (block D)

  The block D estimates the error function. It computes the module of the difference between the neuron output current and the output current of the transconductor that codifies the target information.



M. Valle



Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

13

The current memory cell (block MC)

  The current memory cell is used to store the current that codifies the value of the error function before and after the weight perturbation, i.e. the current $I_{\Delta \varepsilon}$.



M. Valle

Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning


14

The error gradient measure (block EGM)

The EGM block provides to each synapse the sign of the gradient V_{sign} and the gates voltages of the diode connected transistors carrying the current coding the absolute value of the error function gradient ($I_{\Delta \varepsilon}$).

The inputs of the EGM block are:

 - the current value coding the error gradient before the weights perturbation (i.e. $I_{\Delta \varepsilon}(\text{nopert})$)
- the current value coding the error gradient after the weights perturbation (i.e. $I_{\Delta \varepsilon}(\text{pert})$).



M. Valle


Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

15

Simulation results

Function	Number of layer N	Network topology	Input bias	Number of synapses	Pattern presentation time	Vstep [mV]	Time duration of Enable_update [ns]	Convergence	
								#Epoch	Time
Not	1	1x1	0	1	6ms	200	200	10	60ms
And	1	2x1	1	3	6ms	200	100	30	720ms
Or	1	2x1	1	3	6ms	200	100	30	720ms
Ex-Or	2	2x2x1	1+1	9	6ms	20	100	800	19.2ms

 

M. Valle

Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

16

Conclusions (1)

	Computational density [CUPS/mm ²]	Energy efficiency [CUPS/mW]
[Lehmann94]	22.5×10^3	13.5×10^3
[Berg96]	1.15	92
[Cauwenberghs96]	8.7×10^3	35×10^3
[Morie99]	20.4×10^3	32×10^3
[Bo00]	216×10^3	106×10^3
This architecture	11×10^6	62×10^6

M. Valle

Low Power Design Techniques and Neural Applications
Barcelona, Feb. 23-27 2004

Analog on-chip WP learning

17