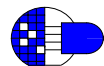




- 1/2. Analog design & Process assessment with Gm/Id
3. Output conductance (V_{ea}), intrinsic capacitances
4. OTA design for low-voltage low-power applications

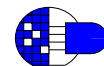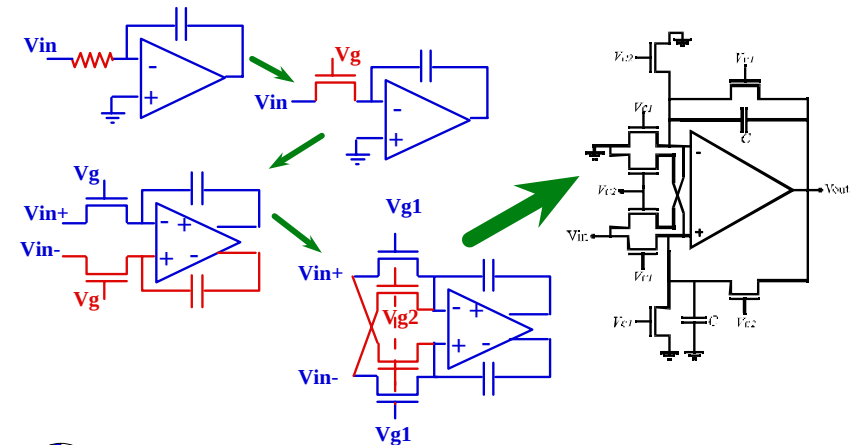5. Harmonic distortion: MOSFET-C filters


- + Switches: SC - ADC
- + Bandgap / voltage references
- + Microsystems



First-Order Mosfet-C Continuous time filter



Continuous-time MOSFET-C

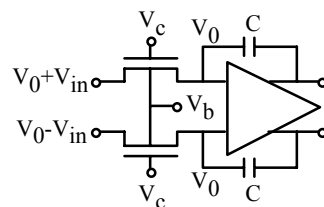

$$R \rightarrow \text{MOS } (R_{on} \div V_c, V_0)$$


$$V_{in} = A \cdot \sin(\omega \cdot t)$$

$$(\text{bulk}) I_D \div V_{in}, V_{in}^2, V_{in}^{3/2}$$

Harmonic distortion (odd $\div \gamma$)

best candidate for low-voltage low-power continuous-time filter implementations with optimal dynamic range



SOI ?

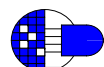


1-T

$$V_C = V_{thf} + GVO$$

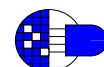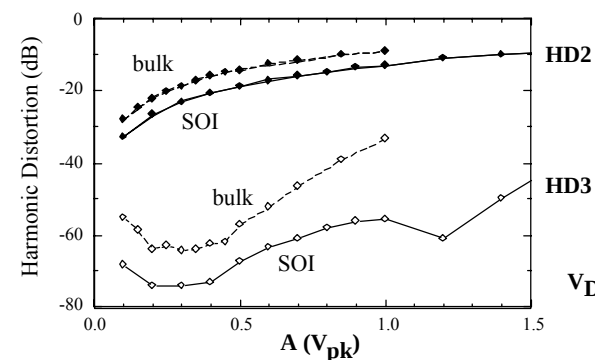
$$V_{in} = V_{DC} + A \cdot \sin \omega t$$



4-MOSFET structure

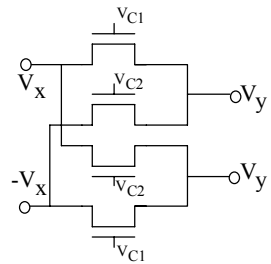

HD3 lower than 2-MOS
HD3 lower in FD SOI

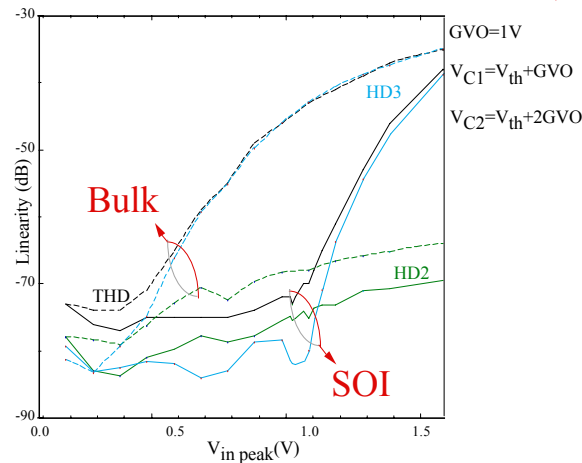

Microelectronics Laboratory

D. Flandre



First-order realization

Frequency response of the filter (influence of Temperature)

The increase
of the Temperature
lowers the mobility

The equivalent
MOS resistor
increases

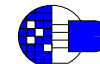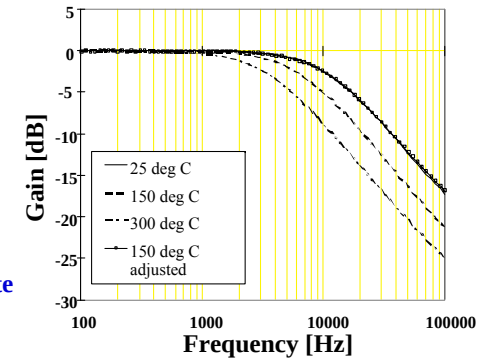On-Chip automatic
tuning to compensate
pole variations




Microelectronics Laboratory

D. Flandre

Harmonic distortion of the filter (influence of Temperature)

THD dominated by HD2

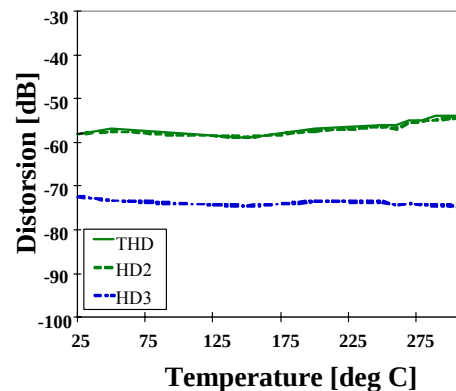Fully differential
architecture to eliminate
even order distortion




Microelectronics Laboratory

D. Flandre

1. Analog design & Process assessment with G_m/I_d
2. Output conductance (V_{ea})...
3. OTA design for low-voltage low-power applications
4. Filters

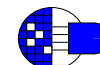5. Switches: SC - ADC

+ Bandgap / voltage references
 + Microsystems




Microelectronics Laboratory


D. Flandre

CMOS analog switch

Lowest V_{dd} for analog :

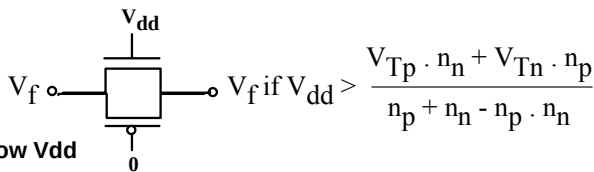

Gap problem for low Vdd

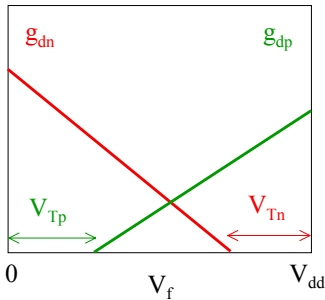



	n_p	n_n	V_T	$V_{dd,min}$
Bulk	1.5	0.7	3.0	
SOI	1.1	0.7	1.7	
	1.1	0.4	1.0	



CMOS analog switch


min device size + $R_{on} < 50\text{ k}\Omega$

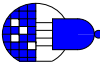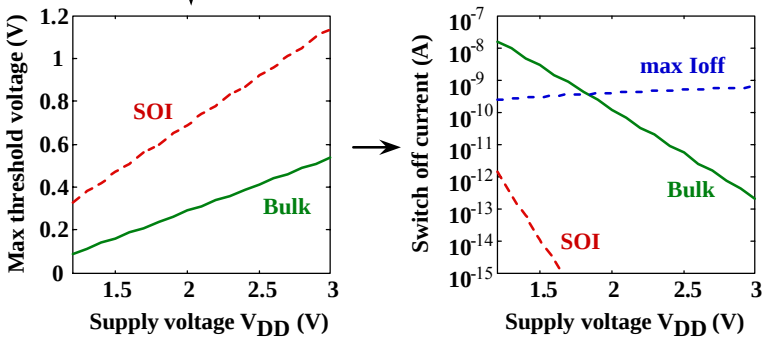(settling error - 0.01% for 500 kHz and 2 pF)



Switch applications

Second-order Sigma-Delta A/D Modulator

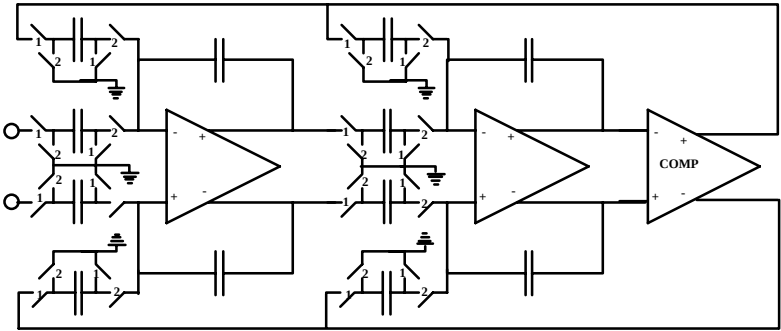

Architecture




Switch applications

Second-order Sigma-Delta A/D Modulator

Temperature	30-250 °C	300 °C
Sampling Frequency	1 MHz	1 MHz
OSR	64	64
Dynamic Range	11 bits @30°C	9 bits
	10 bits @250°C	
Peak SNR	55 dB at RT	30 dB
Supply Voltage	5 V	5 V

Measurement results

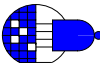

1. Analog design and Process assessment with G_m/I_d
2. Output conductance (V_{ea})...
3. OTA design for low-voltage low-power applications
4. Filters
5. Switches: SC - ADC


6. Bandgap / voltage references

ULP circuit techniques: diodes, charge-pump

+ Microsystems



Structure

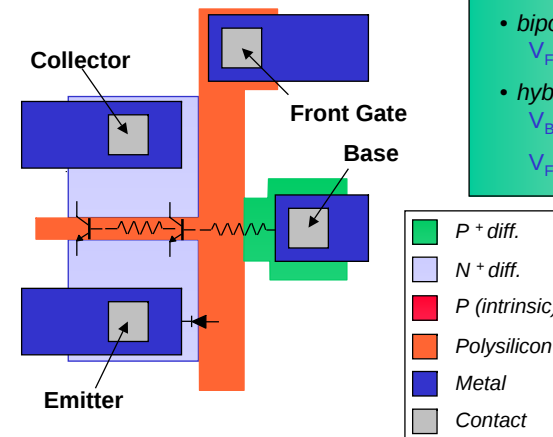

8 μm x 1 μm


Two configurations :

- *bipolar mode* :
 $V_{\text{Front Gate}} = V_{\text{Back Gate}} = 0 \text{ V}$
- *hybrid mode (BCG)* :
 $V_{\text{Back Gate}} = 0 \text{ V}$
 $V_{\text{Front Gate}} = V_{\text{Body}}$



Performances

Current gain from 25°C to 300°C

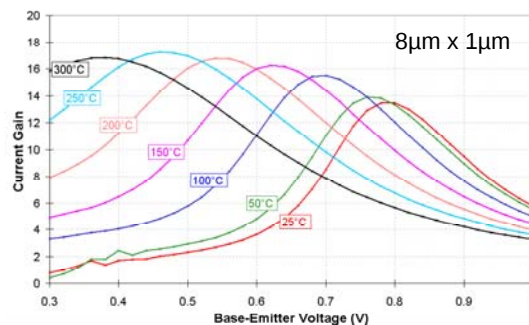


- ▶ Current Gain : 13 @ 25°C
17 @ 300°C
- ▶ Early Voltage : 10...20V
- ▶ Base resistance : 3...5k Ω
- ▶ Good temperature linearity of V_{BE} (slope : -1...-1.5mV/°C)




Bandgap circuit design

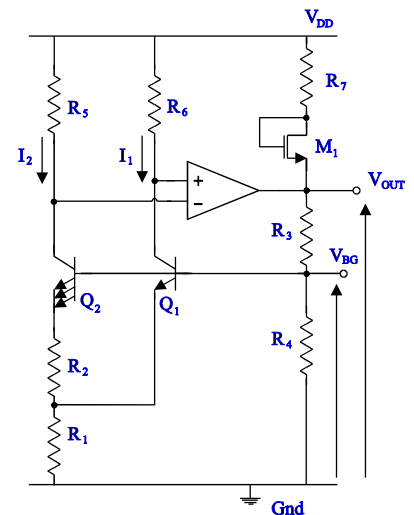- ▶ $V_{\text{bandgap}} = V_{BE} + V_{PTAT}$
- ▶ Design based on measurements
- ▶ single-stage OTA : negative feedback
- ▶ Supply Voltage : 4V to 5V
- ▶ Output Voltages : 1.2V & 3V



Experimental results


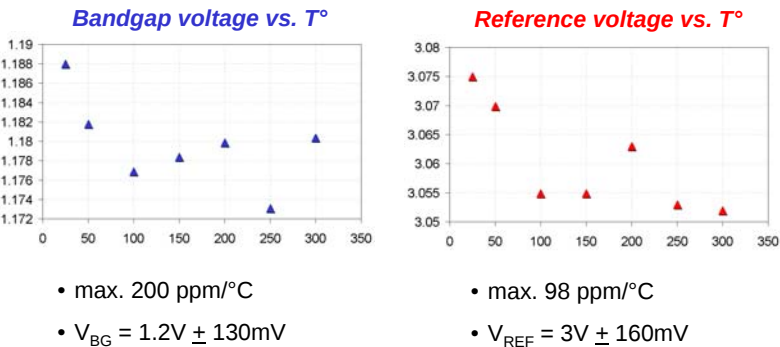


$I_{cons} = 200\mu A$ Area = 0.385mm²

Fairly stable voltage over a very wide temperature range



A new Ultra-Low-Power (ULP) circuit

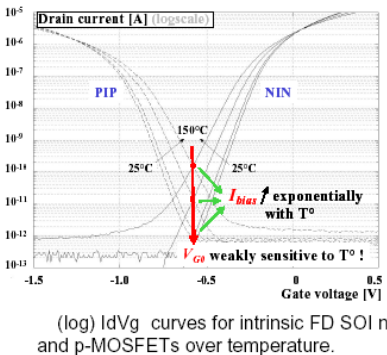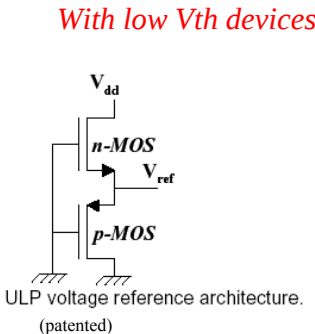


... also for new diode, SRAM, charge-pumps concepts with ultra low leakage !



New Ultra-Low-Power (ULP) circuit

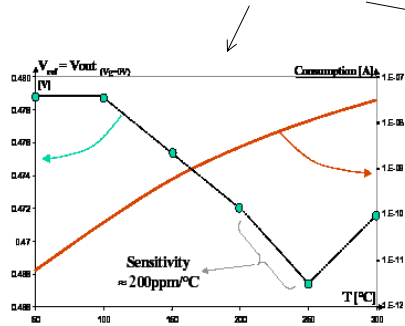Low V_{th} MOS implementation vs bipolar bandgap




	ULP volt. ref	Bandgap ^[1]
Operating T°	25...300°C	25...300°C
V_{dd} - V_{ss}	>0.6V	4...5V
Current consumpt.	1p...20nA (300°C)	200 μA
Output voltage	0.47V (NIN-PIP)	3V $\pm$ 160mV
Output drift	200ppm/°C	100ppm/°C
Active chip area	0.002mm ²	0.385mm ²

Performances comparison between the ULP voltage reference and a bandgap circuit.




Other V_{ref} with multiple- V_{th} process

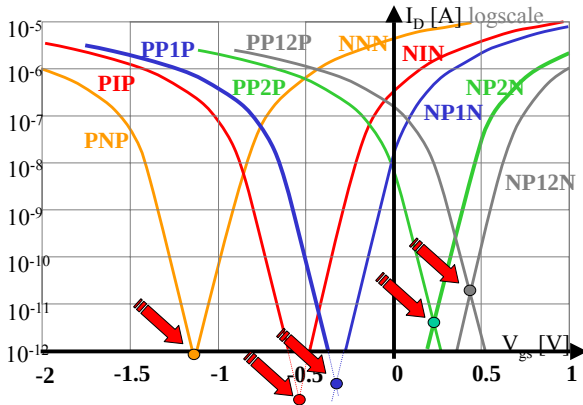I_d - V_{gs} characteristics after optimal doping mask use (UCL FD-SOI process, V_{bs} =0V, 20°C, V_{ds} =1V, W/L =1/3)




More V_{th} without process change ? ...Multi- V_{th}

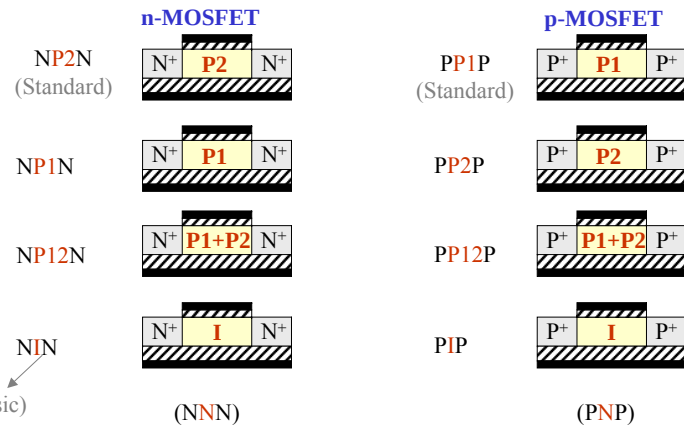Idea: Permute/Add/Remove channel doping by intelligent use of existing masks.




ULP circuit techniques

Reverse ULP diode

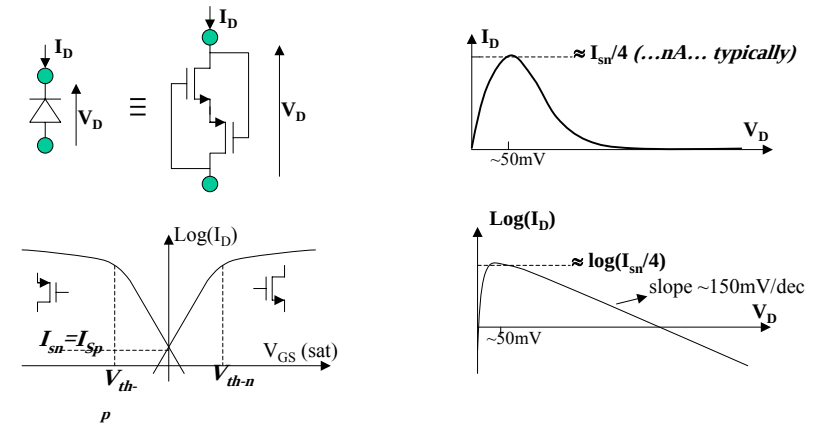


ULP circuit techniques

Classical MOS Diode

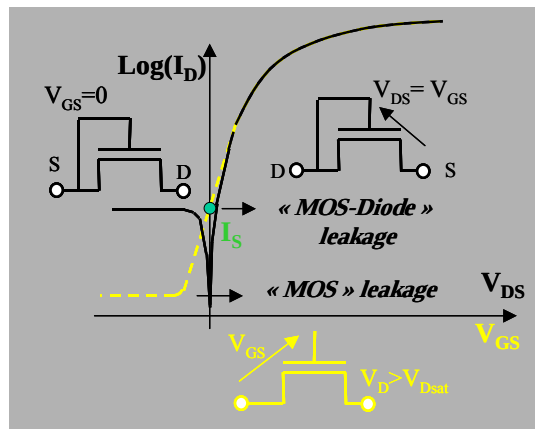



Large reverse leakage current for low V_{th} !

ULP circuit techniques


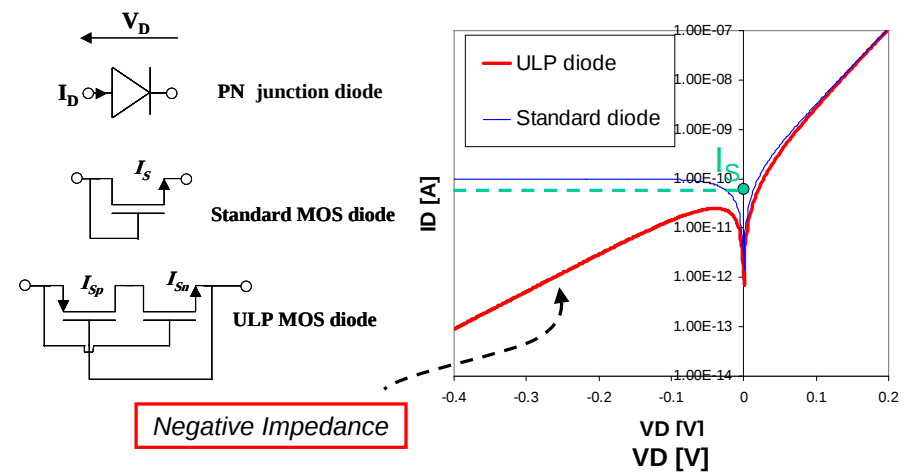


Negative Impedance


ULP Memory Cell

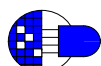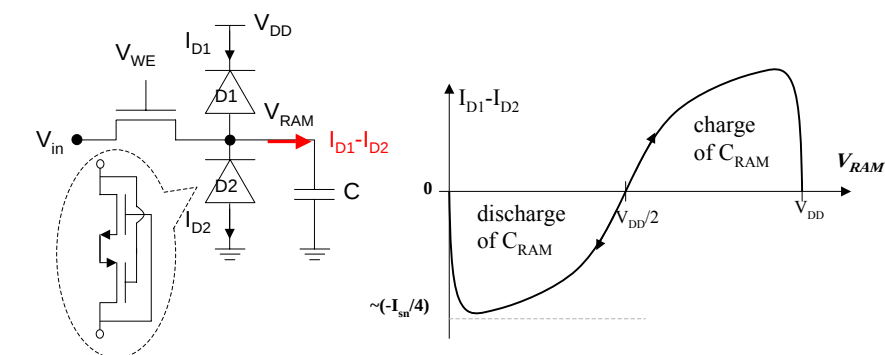




Static Consumption

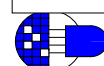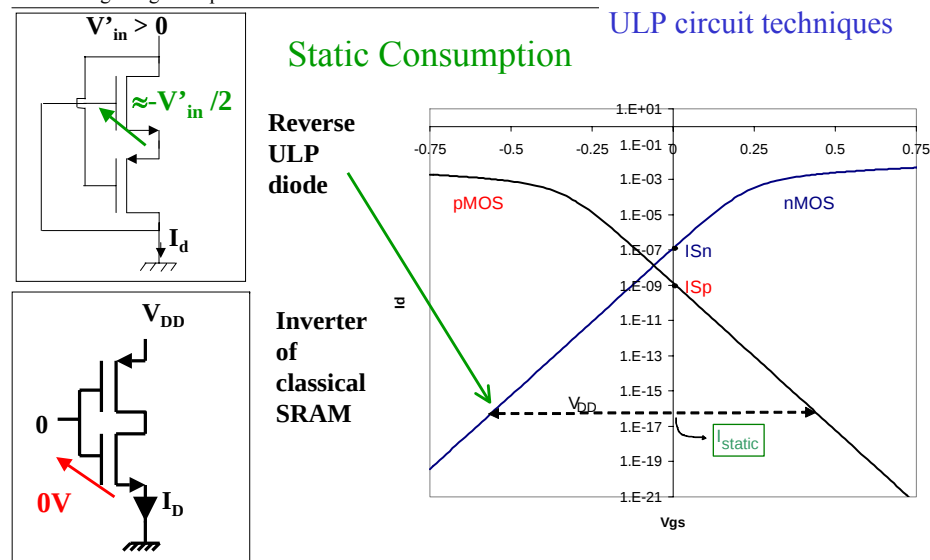

High Temperature Behavior

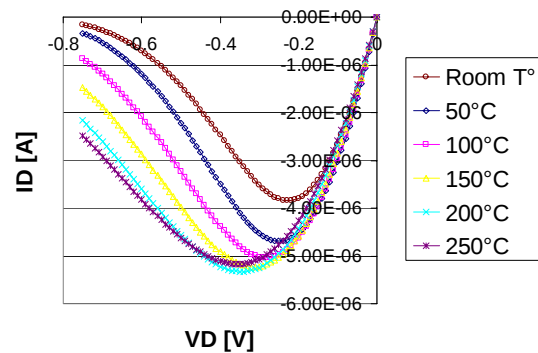


I-V characteristics of a ULP diode featuring NIN n-MOSFETs and PP12P p-MOSFETs with $W=9\mu\text{m}$ and $L=2\mu\text{m}$

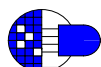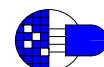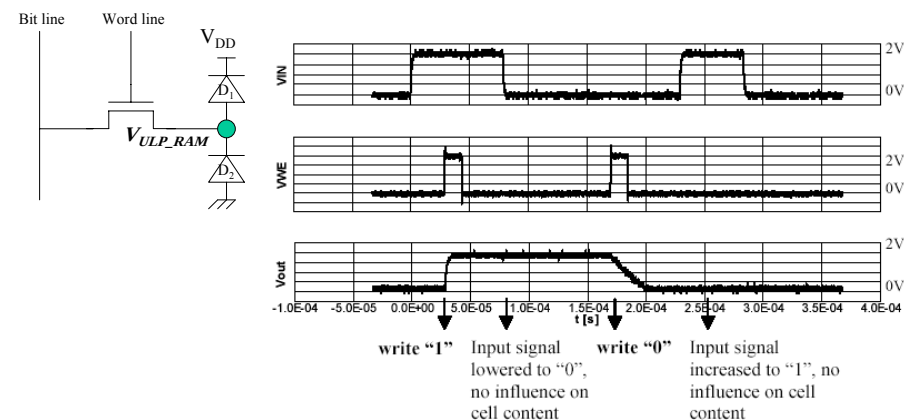
ULP Memory Functionality up to 280°C 

Charge pump



- Based on Dickson's

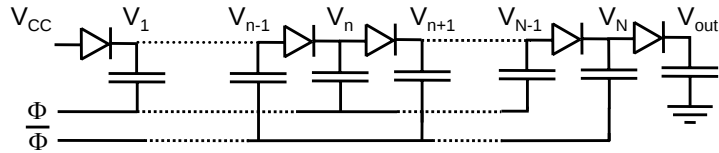
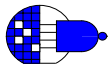
$$\text{Final voltage} = \text{supply voltage} + \left[N \times f\left(\frac{\Phi - V_D}{\lambda}\right) \right]$$



- Design of 3x with MOS

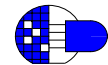
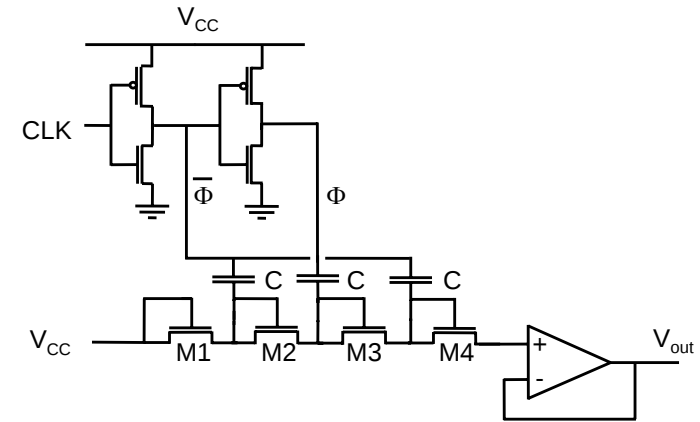


- Specification :
 - » Supply Voltage = 1.8 V
 - » Programming voltage = 5 V
- SOI vs. bulk



Body effect

$n_{\text{SOI}} = 1.1$

$n_{\text{bulk}} = 1.5$

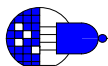
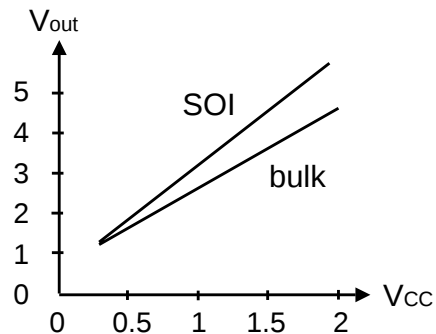


- Experimental results

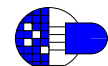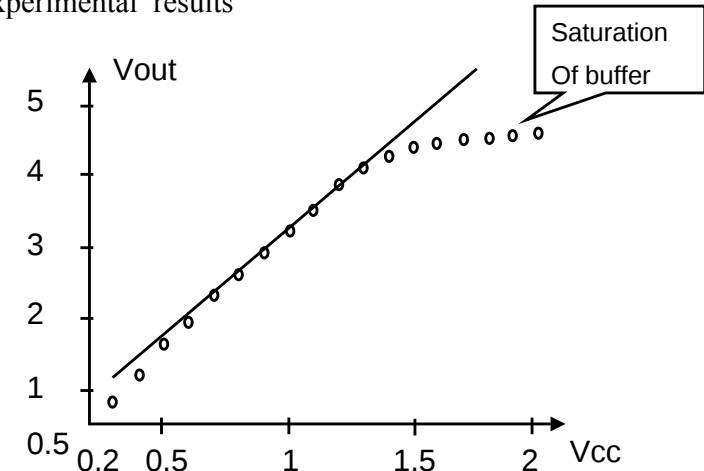



Charge-pump

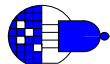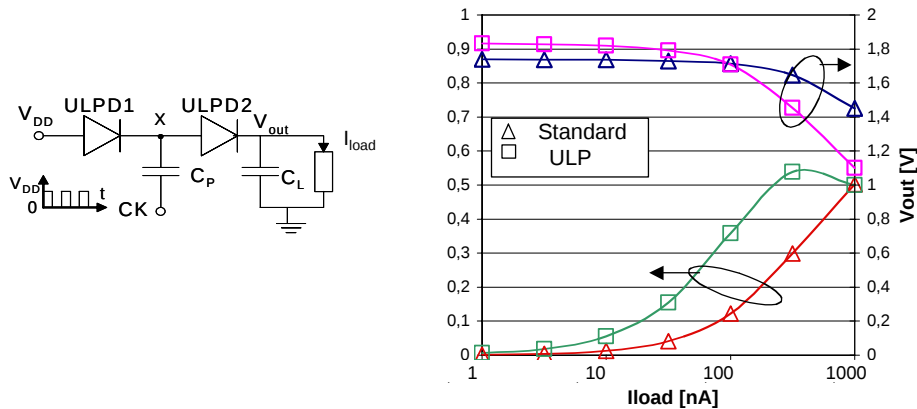Voltage doubler with standard MOS and ULP diodes



Charge-pump


High-temperature behavior

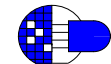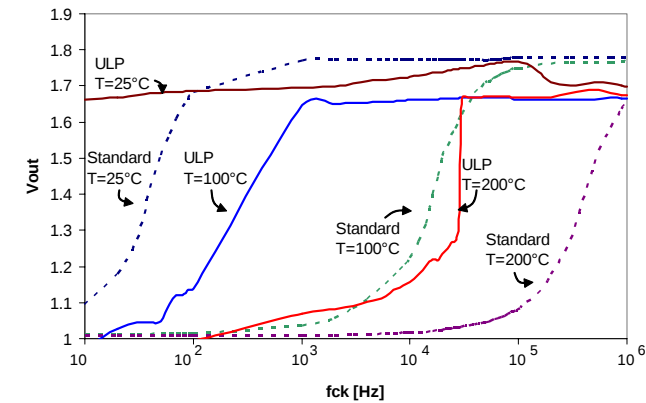

Outline



1. Analog design & Process assessment with G_m/I_d
2. Output conductance (V_{ea})...
3. OTA design for low-voltage low-power applications
4. Filters
5. Switches: SC - ADC
6. Bandgap / voltage references, ULP circuit techniques

7. Heterogeneous microsystems


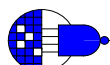


Microsystems

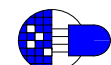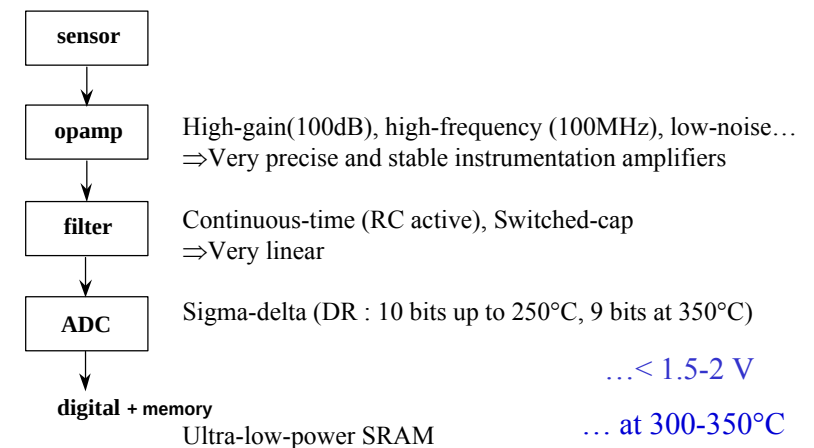Towards fully integrated sensing chain...




Smart SOI sensor

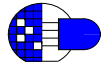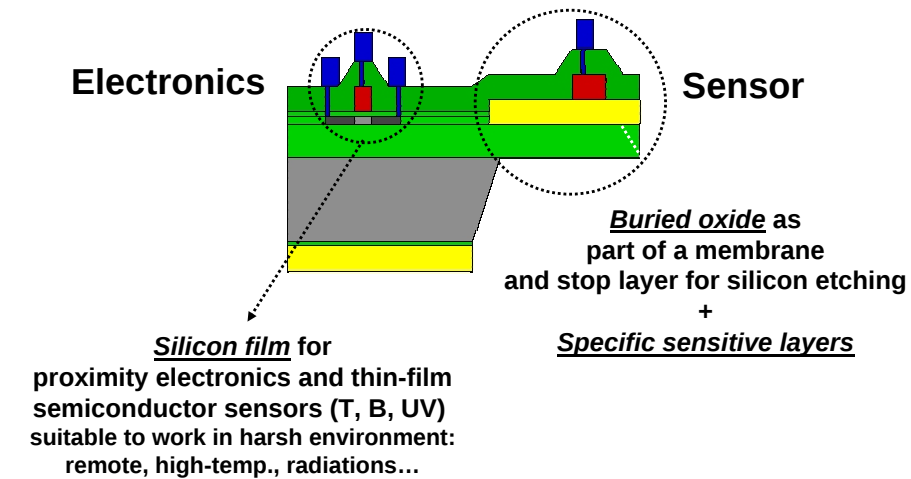

Microelectronics Laboratory

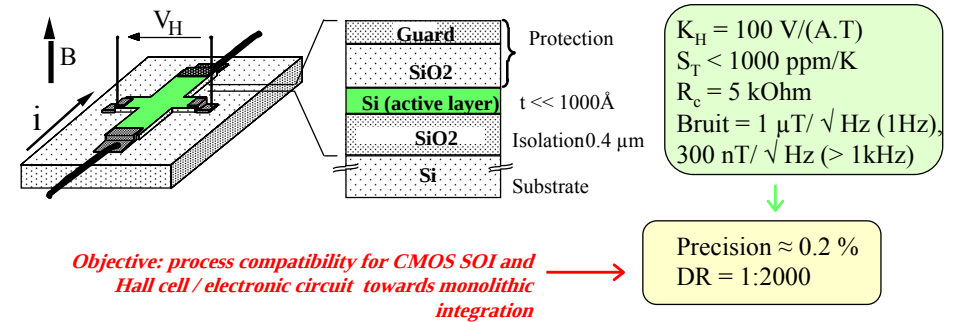D. Flandre


Development of a SOI based Hall Effect sensor for an electricity meter



EUREKA project:

Schlumberger Industries (Coordinator) - France
 Université de Montpellier II - France
 Ecole Polytechnique Fédérale de Lausanne (EPFL) - Switzerland

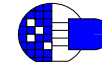Microélectronique Marin (EMMARIN) - Switzerland
 Université catholique de Louvain-la-Neuve (UCL) - Belgium
 Crouzet Automatismes - France



Microelectronics Laboratory



D. Flandre

Bulk micromachining

Si etch with TMAH ou Tetramethylammonium hydroxyde

On standard SOI wafers => Sandwich: $1 \mu\text{m SiO}_2 / \text{Si}_3\text{N}_4 \text{ LPCVD} / \text{SiO}_2$


Differential Piezoresistive structure

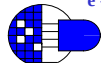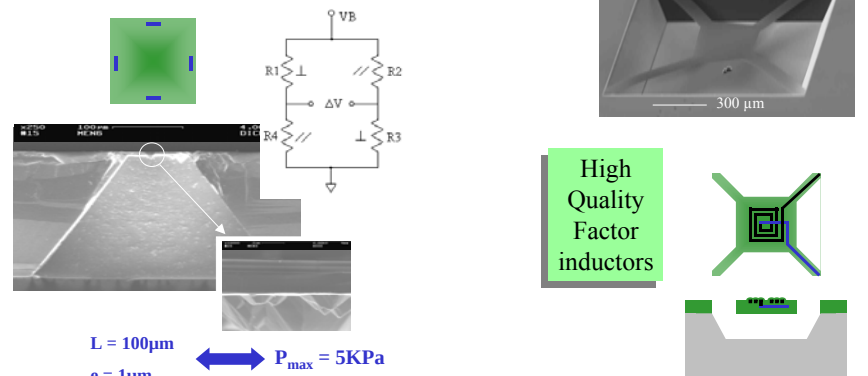

Microelectronics Laboratory

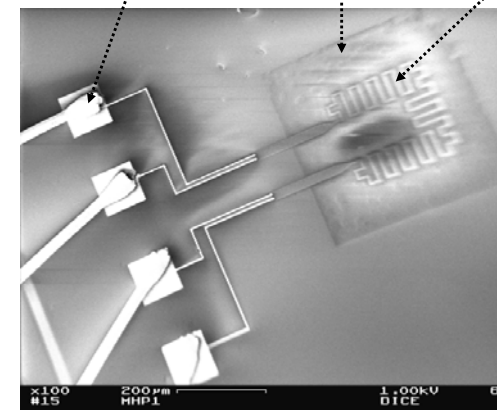
D. Flandre

4 contacts membrane Polysilicon loop shape



- ✓ low cost
- ✓ very low consumption (20 mW at 400°C)
- ✓ high insulation (20.000 °C/W)
- ✓ high thermal uniformity

Applications : Gas, Flow, IR sensors...


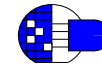


Microelectronics Laboratory

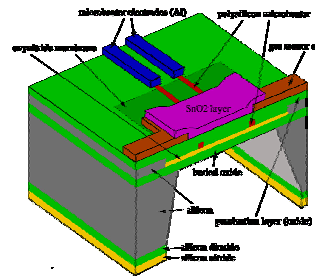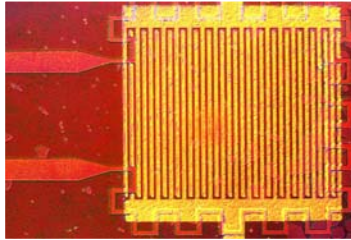D. Flandre

The resistivity of a sensitive layer (as SnO_2 or WO_3) changes in presence of gases at 250 - 350°C


Microheater + interdigitated Au electrodes + sensitive layer



Co-integration of CMOS circuits and sensors,
in compatible technologies, on same Si die

Goals: compacity, cost, performance


Example processed in UCL (DICE):

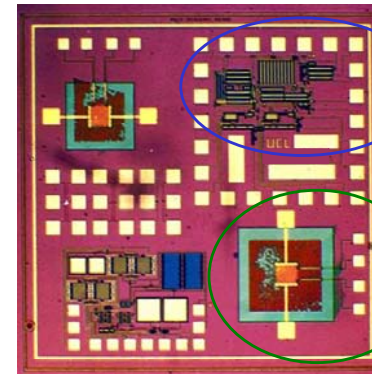

CMOS on silicon on insulator:
- analog circuits : Micropower, RF (1 GHz),
Or High temperature (300-350°C)
- sensors: temperature, magnetic (Hall effect), optical (UV)

Sensors on membranes:

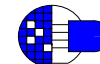- Gas
- Pressure
- Flow
- Thermopiles (IR)...



- *Generic High-performance Fully-Depleted SOI CMOS*
- *Easy integration of special devices, sensors, MEMS*
- *Operation in harsh conditions (micropower, high-temperature, remote RF link...)*
- *Broad applications: automotive, aerospace, wireless sensors, biomedical, quality control...*
- *« Green energy » or « Energy scavenging »: autonomy*

